

Digital IC Comprehensive Experiment Report

Zhou Zixuan 2200012728

Experiment Name: 16-bit High-Speed Adder Design

Experiment Objective

Familiarize with digital integrated circuit design and simulation methods to implement functional circuits.

Experiment Content

- First, complete the circuit design and simulation of a **16-bit Ripple Carry Adder (RCA)** as a reference circuit and measure the **maximum delay time** as the speed benchmark for this experiment.
- Design a **16-bit high-speed adder** and achieve a speed improvement of more than **2x** through optimization of **adder structure, circuit design, and device sizing**.

Experiment Steps

1. Construct the 16-bit Ripple Carry Adder (RCA) circuit

- Simulate and measure the **maximum delay**.


2. Design a 16-bit High-Speed Adder (Carry Select Adder)

- Modify the MOS transistor sizes in the full adder so that **all MOS transistors have $W/L = 200n/40n$** .
- Connect the modified full adders in series to form a **4-bit RCA**.
- Construct a **MUX**, where **all PMOS have $W/L = 200n/40n$** and **all NMOS have $W/L = 120n/40n$** , used for selection.
- Use **two 4-bit RCAs** and **five MUXes** (for selecting **S0, S1, S2, S3, and Co**) to form a **4-bit Carry Select Adder**, with the **Ci** of the two 4-bit RCAs connected to **VDD** and **GND**, respectively.
- Use **three 4-bit Carry Select Adders** and **one 4-bit RCA** to construct a **16-bit Carry Select Adder**.
- Measure the **maximum delay**.
- **Draw the layout**.

- Perform post-layout simulation to verify correct functionality.


Experiment Results & Analysis


1. Full Adder

 

- All PMOS: W/L = 400n/40n
- All NMOS: W/L = 200n/40n

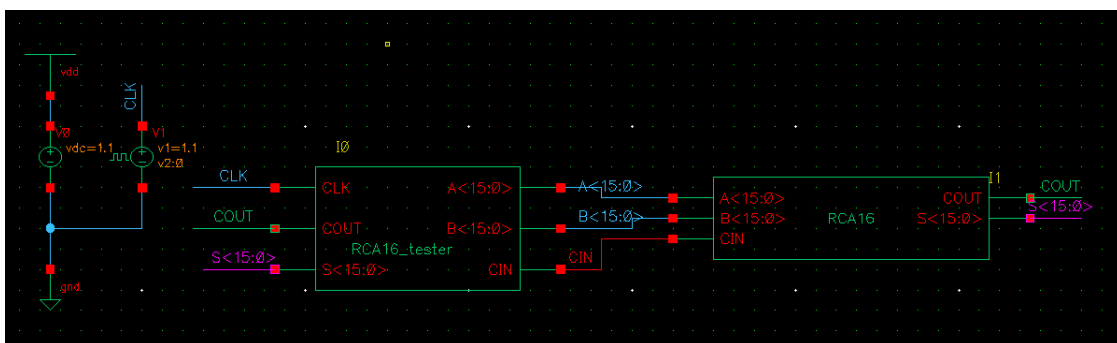
2. RCA Test Circuit & Maximum Delay Measurement



 


- Measured Maximum Delay:
 - $3.83585 \text{ ns} - 3.09474 \text{ ns} = 0.7411 \text{ ns} = 741.1 \text{ ps}$

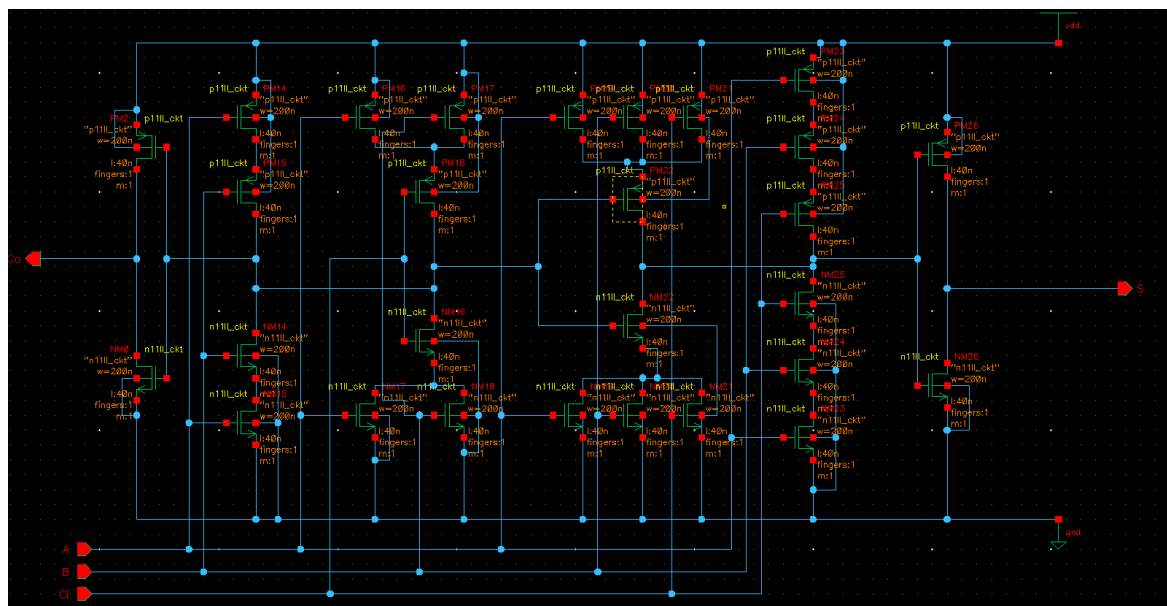
3. Modified Full Adder (Circuit connections remain unchanged)




- Constructed 4-bit RCA circuit

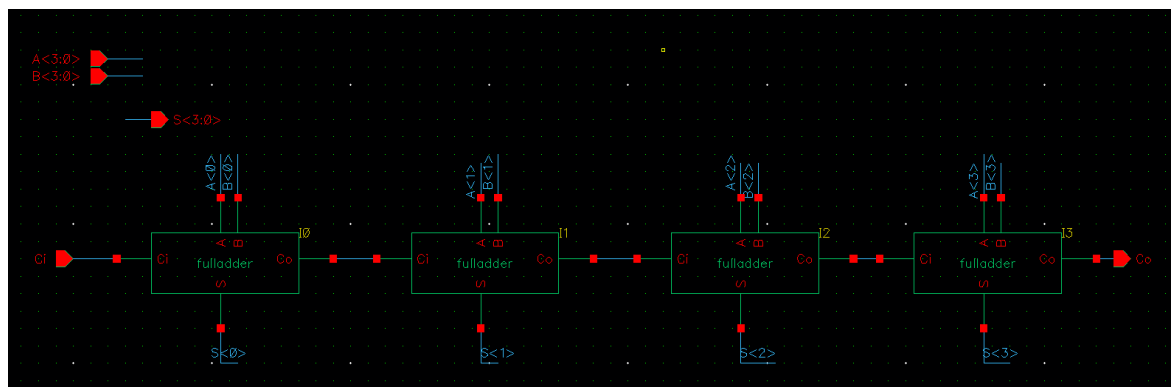


- Designed **MUX** circuit

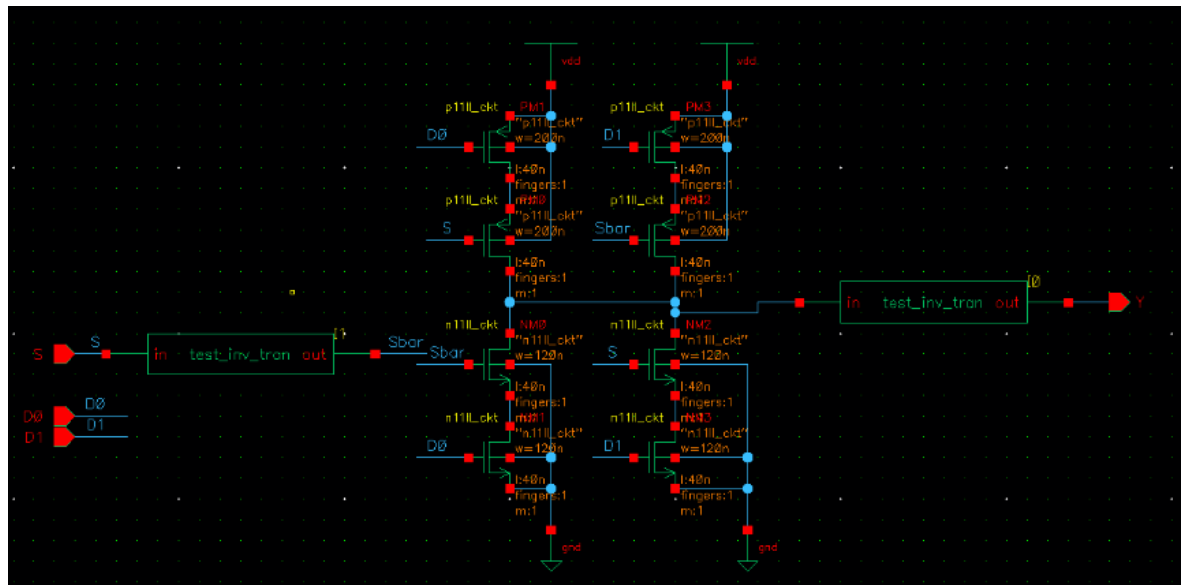

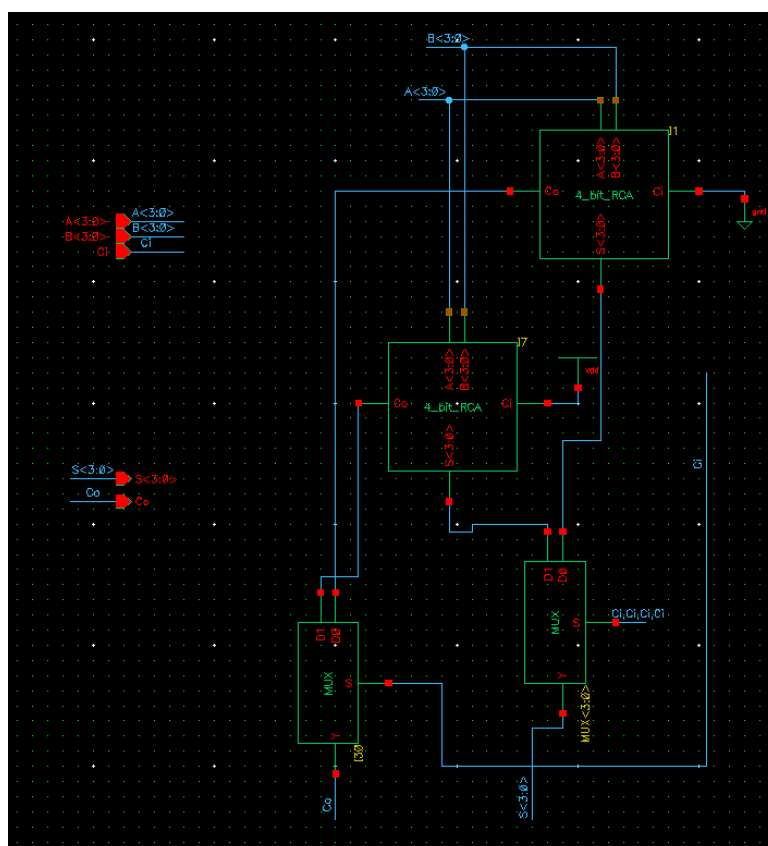
- Built 4-bit Carry Select Adder using 4-bit RCA and MUX



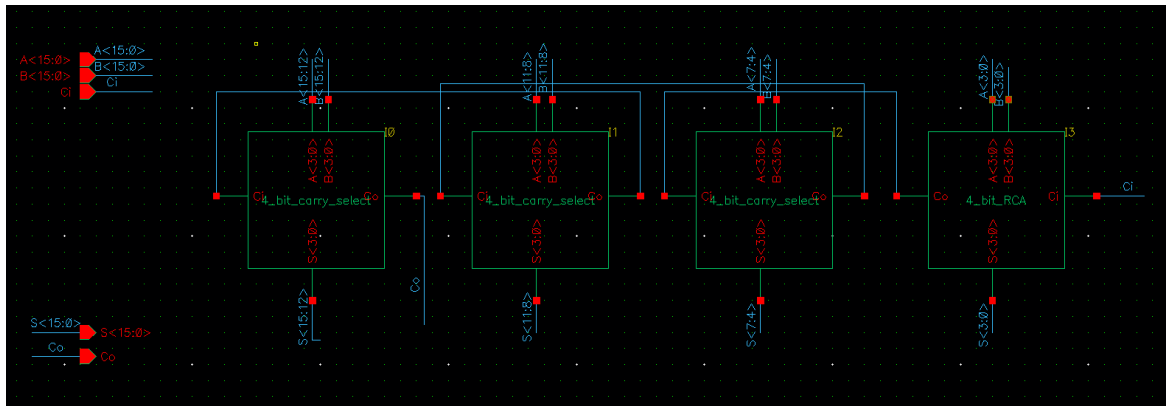
- Connected **one 4-bit RCA** and **three 4-bit Carry Select Adders** to form a **16-bit Carry Select Adder**



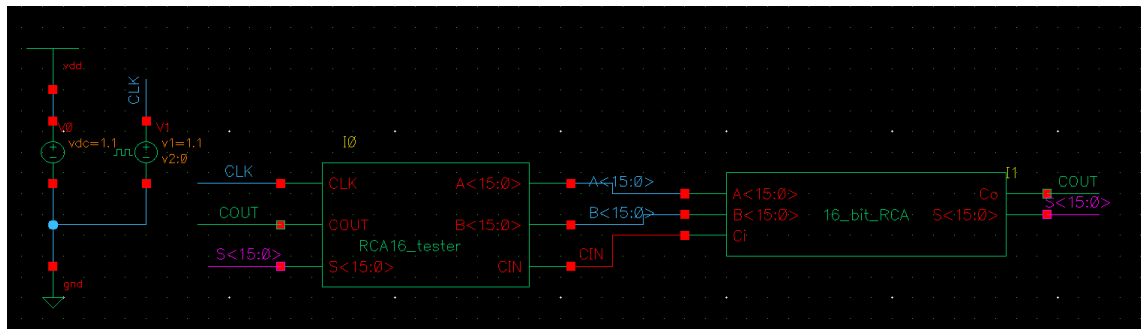4. Optimized Circuit & Pre-layout Simulation Results



 
- Optimized Pre-layout Delay Measurement:




- 3.4642 ns - 3.09496 ns = 0.3692 ns = 369.2 ps
- This meets the design goal: 369.2 ps < (741.1 ps / 2) = 370.55 ps

5. Layout Design


- Full Adder Layout

 


- 4-bit RCA Layout

 


- MUX Layout

 

- 4-bit Carry Select Adder Layout

 


- 16-bit Carry Select Adder Layout

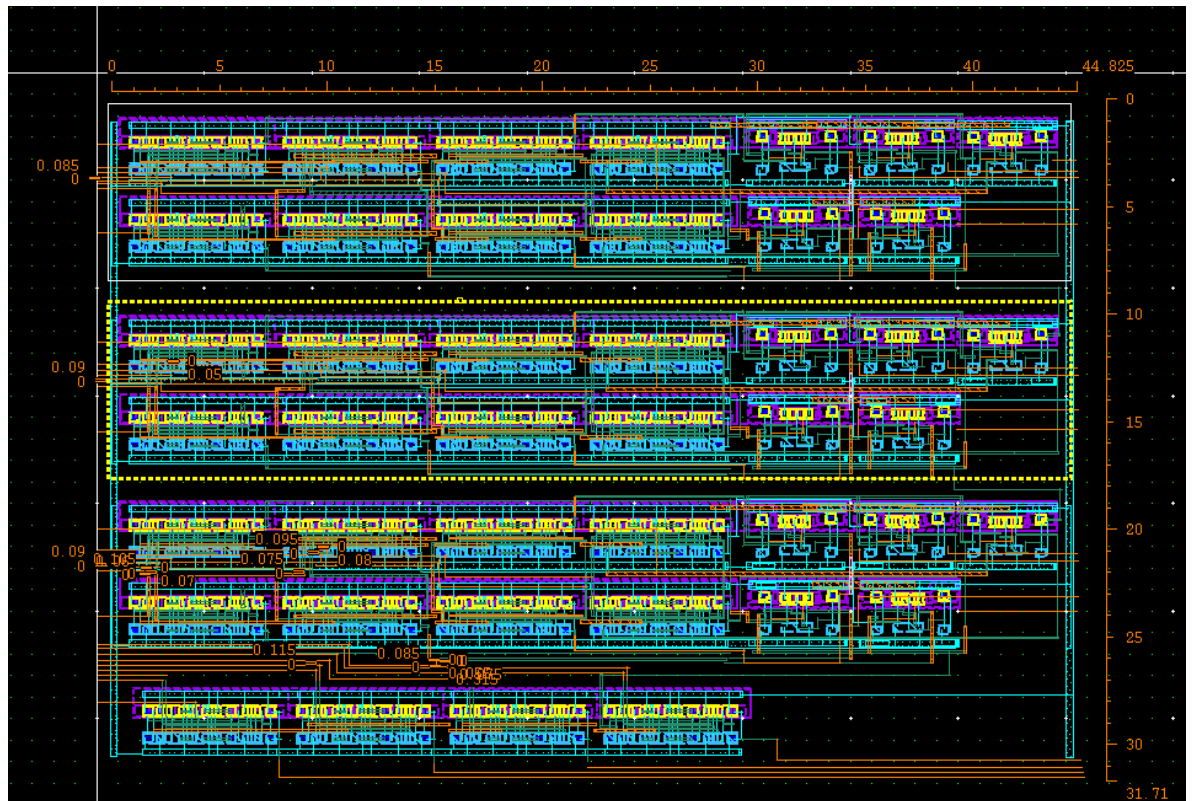


- Input connections from the left, output connections from the right
- Overall layout aspect ratio: $44.825 \mu\text{m} / 31.71 \mu\text{m}$, meeting the requirements

6. Design Rule Check (DRC) & Layout vs. Schematic (LVS) Results

- DRC Passed

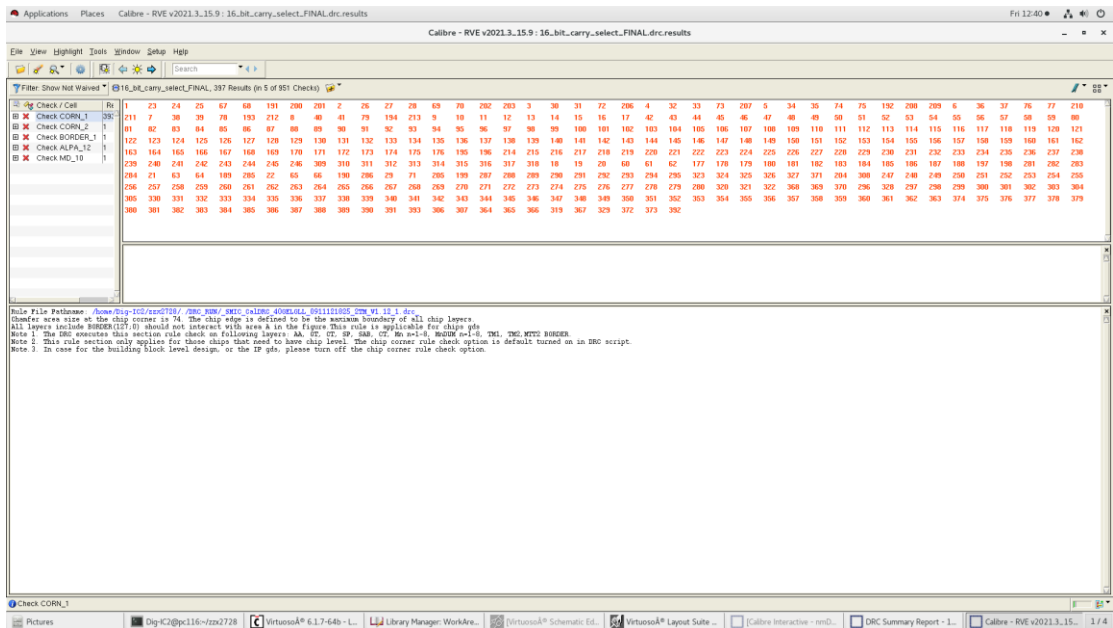

- LVS Passed

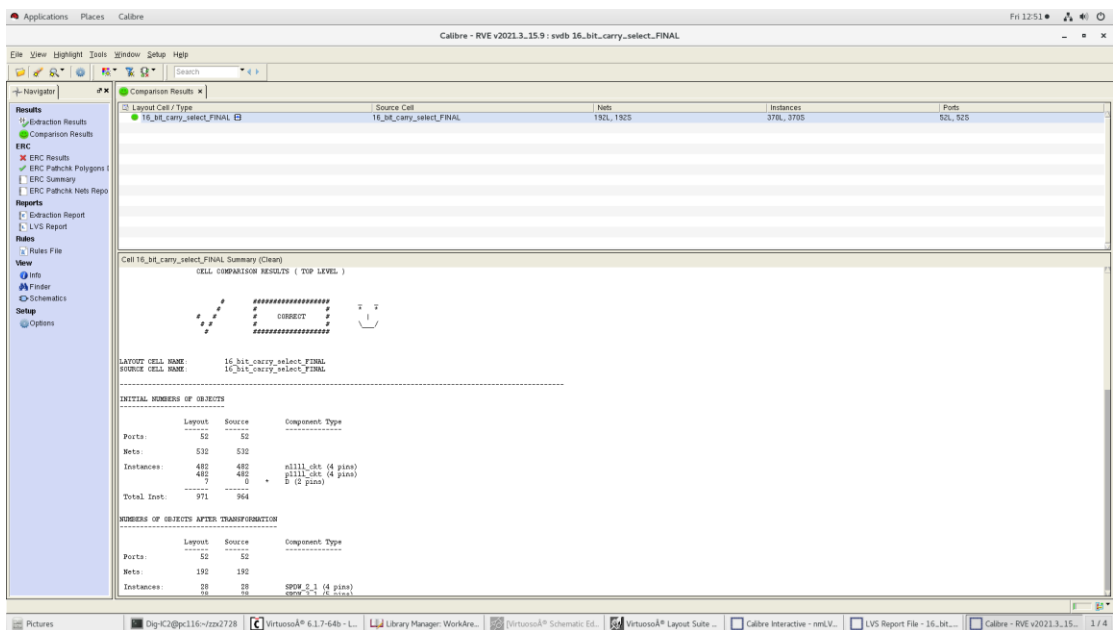

7. Post-layout Simulation & Final Validation

- Delay Analysis Post-layout:



```

tran: time = 814.4 ps (4.07 %), step = 400 ps (2 %)
tran: time = 1.614 ns (8.07 %), step = 400 ps (2 %)
tran: time = 2.722 ns (13.6 %), step = 307.8 ps (1.54 %)
[3.04501 ns] A 0 + B 0 + CIN 0 = sum1 0 | 0 sum2 = S 0 + CO 0
----- error_count = 0
tran: time = 3.503 ns (17.5 %), step = 3.597 ps (18 m%)
tran: time = 4.554 ns (22.8 %), step = 63.81 ps (319 m%)
tran: time = 5.696 ns (28.5 %), step = 369 ps (1.84 %)
tran: time = 6.791 ns (34 %), step = 400 ps (2 %)
tran: time = 7.591 ns (38 %), step = 400 ps (2 %)
tran: time = 8.711 ns (43.6 %), step = 319.4 ps (1.6 %)
[9.04501 ns] A 0 + B 65535 + CIN 1 = sum1 65536 | 65536 sum2 = S 0 + CO 65536
----- error_count = 0
tran: time = 9.502 ns (47.5 %), step = 6.53 ps (32.7 m%)
tran: time = 10.55 ns (52.7 %), step = 159.6 ps (798 m%)
tran: time = 11.73 ns (58.7 %), step = 265.6 ps (1.33 %)
tran: time = 12.77 ns (63.8 %), step = 388.2 ps (1.94 %)
tran: time = 13.57 ns (67.8 %), step = 400 ps (2 %)
tran: time = 14.7 ns (73.5 %), step = 330.3 ps (1.65 %)
[15.045 ns] A 10482 + B 17931 + CIN 0 = sum1 28413 | 28413 sum2 = S 28413 + CO 0
----- error_count = 0
tran: time = 15.51 ns (77.5 %), step = 10.28 ps (51.4 m%)
tran: time = 16.56 ns (82.8 %), step = 235.3 ps (1.18 %)
tran: time = 17.69 ns (88.5 %), step = 400 ps (2 %)
tran: time = 18.79 ns (94 %), step = 400 ps (2 %)
tran: time = 19.59 ns (98 %), step = 400 ps (2 %)
Number of accepted tran steps = 633

Notice from spectre during transient analysis 'tran'.
Trapezoidal ringing is detected during tran analysis.
Please use method=trap for better results and performance.

Initial condition solution time: CPU = 763.769 ms, elapsed = 763.787 ms.
Intrinsic tran analysis time: CPU = 23 s, elapsed = 23.0613 s.
Total time required for tran analysis 'tran': CPU = 23.9862 s, elapsed = 24.0476 s.
Time accumulated: CPU = 25.632 s, elapsed = 25.8819 s.

```

- The design functions correctly, and the error count is zero.

Conclusion

The **16-bit Carry Select Adder** achieved over **2x speed improvement** compared to the **Ripple Carry Adder**, successfully meeting the experimental goals. The design was verified through **circuit simulation, layout verification (DRC, LVS), and post-layout validation**, confirming that the high-speed adder performs correctly.